

## How to draw a circuit

Scientists use symbols to draw circuits

A bulb (called a lamp)  
looks like this:



A battery (called a cell)  
looks like this:



And a switch looks like this:




open (off)



closed (on)

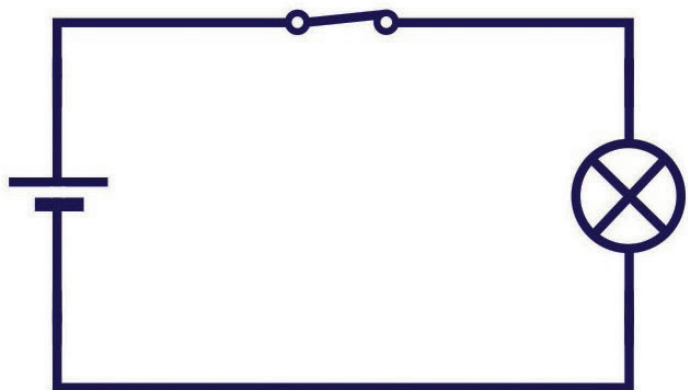So our circuit would be  
drawn like this:



---

## How to draw a circuit

Scientists use symbols to draw circuits

A bulb (called a lamp)  
looks like this:



A battery (called a cell)  
looks like this:



And a switch looks like this:



open (off)



closed (on)

So our circuit would be  
drawn like this:

